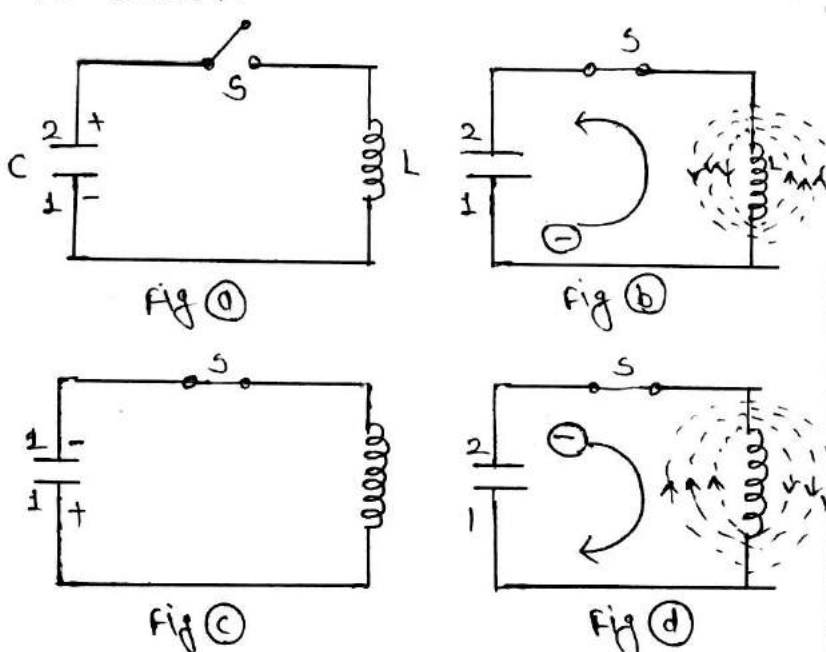


SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	a) ANS:	<p>Explain concept of oscillations on LC Tank circuit.</p>  <p>Fig (a) Fig (b)</p> <p>Fig (c) Fig (d)</p> <p>A circuit which produces electrical oscillations of any desired frequency is known as an oscillatory circuit. This circuit consists of two reactive elements namely inductor L and capacitor C connected in parallel with each other as shown in Fig (a) thus such a circuit is also known as LC Tank circuit. An inductor stores energy in its magnetic field whenever current flows through it.</p>	<p>correct figure 2 Marks valid description 2 Marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 1	a)	<p>similarly capacitor stores energy in its electric field, whenever a voltage is applied across its plates.</p>	
	Ans:	<p>suppose capacitor has been charged from a dc voltage source with polarity as shown in fig (a) as the switch S is open it cannot discharge through the coil (L)</p> <p>When switch is closed as shown in fig (b) the capacitor discharge through the coil L. The discharging due to the flow of electrons from plate 1 to 2 through coil (L) indicated by the arrow. This current flow sets up magnetic field around the coil. This magnetic field stores the energy released by the electric field. At this instant the electrical energy stored in the capacitor becomes zero and the energy stored in magnetic field is max^m.</p> <p>once the capacitor is discharged completely the magnetic field around the coil begins to collapse and produces a counter emf. According to Lenz's law the counter emf keeps the electrons moving in the same dirⁿ as shown in fig (b) This again charges the capacitor though in the opposite direction as show in fig (c) when the capacitor is charged completely in the opposite direction the magnetic</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105




SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	Q	<p>field around the coil is also collapsed completely. At this instant the energy previously stored in the magnetic field has now converted into the energy stored in the electric field of capacitor. After this capacitor starts discharging in the opposite direction so that electrons now move from plate 2 to 1 as shown in fig (d) The electric field start collapsing whereas magnetic field starts building up again but in reverse direction the above mentioned sequence of charging and discharging of a capacitor result in an alternate motion of electrons. As a result of this, energy is alternatively stored in the electric field of the capacitor and magnetic field of the coil. This interchange of energy between capacitor and coil continues to be repeated and results in the production of electrical oscillations.</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

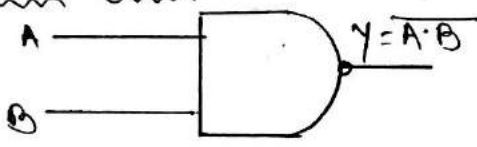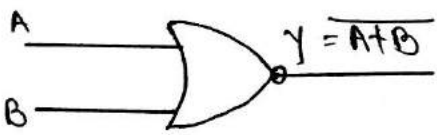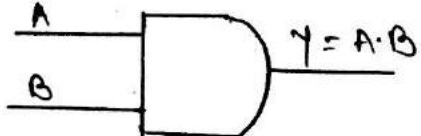
SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME																																																			
Q.1	b7	<p>Draw symbols and truth table of NAND Gate, NOR, AND, OR Gate.</p> <p>Ans:</p> <p>i) <u>NAND Gate</u> →</p>  <p><u>NAND Gate symbol</u></p> <p><u>Truth table</u></p> <table border="1" data-bbox="965 806 1268 1131"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>ii) <u>NOR Gate</u> →</p>  <p><u>symbol of NOR Gate</u></p> <p><u>Truth table</u></p> <table border="1" data-bbox="925 1321 1260 1657"> <thead> <tr> <th colspan="2">Input</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>iii) <u>AND Gate</u> →</p>  <p><u>Truth table</u> →</p> <table border="1" data-bbox="925 1713 1260 2016"> <thead> <tr> <th colspan="2">Input</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	Input		Output	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0	Input		Output	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	<p>For each correct symbol and truth table 1M</p>
A	B	Y																																																				
0	0	1																																																				
0	1	1																																																				
1	0	1																																																				
1	1	0																																																				
Input		Output																																																				
A	B	Y																																																				
0	0	1																																																				
0	1	0																																																				
1	0	0																																																				
1	1	0																																																				
Input		Output																																																				
A	B	Y																																																				
0	0	0																																																				
0	1	0																																																				
1	0	0																																																				
1	1	1																																																				

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

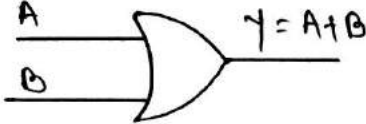SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME																		
Q.4	b)	<p>iv) OR Gate \rightarrow</p>  <p>symbol of OR Gate</p> <table border="1" data-bbox="925 683 1244 996"> <thead> <tr> <th colspan="2">input</th> <th>output</th> </tr> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	input		output	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	
input		output																			
A	B	Y																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	1																			
Q.4	c)	<p>state any four basic laws of Boolean Algebra.</p> <p>Ans:</p> <p>i) Commutative law \rightarrow</p> <p>a) $A + B = B + A$</p> <p>b) $A \cdot B = B \cdot A$</p> <p>ii) Associative law \rightarrow</p> <p>a) $(A + B) + C = A + (B + C)$</p> <p>b) $(A \cdot B) \cdot C = A \cdot (B \cdot C)$</p> <p>iii) Distributive law \Rightarrow</p> <p>a) $A(B + C) = AB + AC$</p>	<p>each correct law 1 Mark.</p>																		

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105



SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	c)	<p>iv) AND law \rightarrow</p> <p>a) $A \cdot 0 = 0$</p> <p>b) $A \cdot 1 = A$</p> <p>c) $A \cdot A = A$</p> <p>d) $A \cdot \bar{A} = 0$</p> <p>v) OR law \rightarrow</p> <p>a) $A + 0 = A$</p> <p>b) $A + 1 = 1$</p> <p>c) $A + A = A$</p> <p>d) $A + \bar{A} = 1$</p> <p>vi) Inversion law</p> <p>a) $\overline{\bar{A}} = A$</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

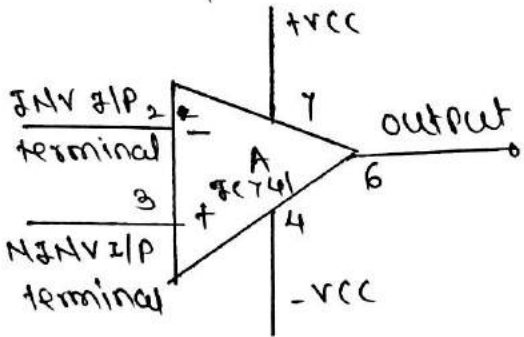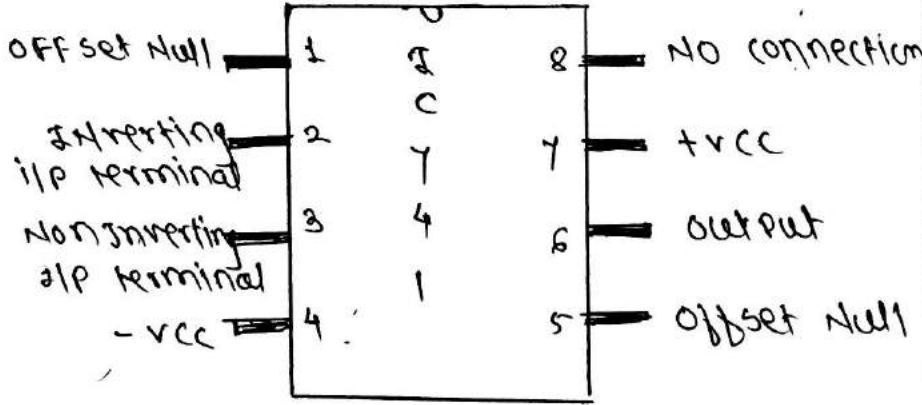SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	d)	<p>Draw symbols and pin diagram of IC 741</p> <p>Ans: </p> <p>symbol of OP-AMP</p>  <p>pin diagram of IC 741</p>	<p>for correct symbol 2 marks</p> <p>for correct pin diag. 2 marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	ex Ans.	<p>state specifications of CRO and function generator (each two)</p> <p>specifications of CRO →</p> <p>a) the vertical sensitivity → It is ratio of voltage applied to vertical deflection plates to the deflection in cm. It is measured as volts/div.</p> <p>b) Input Impedance → This is the impedance offered by the CRO to the given i/p signal. Typical values of these parameter are $1M\Omega$ shunted by 25 pF.</p> <p>c) maximum i/p → This is the max^m value of voltage that can be applied to the given CRO safely. Typical value of max^m i/p voltage = 400Vdc</p> <p>d) Accuracy → The accuracy is expressed in terms of percentage. Typical value of CRO is $\pm 3\%$.</p> <p>e) Bandwidth → This is 3dB bandwidth of vertical ampl^r of CRO. Typical value is 15MHz.</p>	<p>For correct specification of each 2 Marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.1	e)	specification of function generator → 1) make/model 2) power supply - 230V AC, 50Hz 3) calibration accuracy - ±1% under normal conditions 4) display type - Analog/digital $3\frac{1}{2}$ - $3\frac{3}{4}$ 5) freq. range 6) frequency response - within ±0.1% (1KHz ref) over entire freq. range 7) freq. shift - ±15% variation in the volt should not affect freq. of 8) signal generation - sine/square/sawtooth/triangular etc.	
Q.2	f) Ans:	state classification of transducer with one example of each. on the basis of method of transduction A) Active transducer → These are the transducers which do not require any external or auxiliary power source to generate equivalent output i.e. volt or current. They are self generating	For valid classification 4M.

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 7	b)	<p>transducers</p> <p>eg. piezoelectric crystal transducer</p> <p>b) passive transducers → These are the transducers that require external or auxiliary power supply for their operation of conversion of physical quantity into electrical signal</p> <p>eg. measurement of displacement using LVDT and potentiometer.</p> <p>c) Analog transducers → They convert the input physical quantity into analog output which is continuous function of time</p> <p>eg. thermocouple.</p> <p>d) Digital transducer → They convert the input physical quantity into digital form. i.e. in the form of pulses having logic 0 & logic 1</p> <p>eg. Rotary Encoder.</p> <p>e) primary and secondary transducer → sometimes physical quantity is not suitable for direct transduction.</p> <p>eg. pressure measurement using LVDT here first pressure is converted into linear displacement</p>	



GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.7	b)	<p>by using Bourdon Tube and then linear displacement is converted into voltage using LVDT. Here the bourdon tube acts as a primary transducer because it senses pressure and converts it into displacement. which is suitable for LVDT which acts as secondary transducer.</p> <p>→ on the basis of Electrical parameters</p> <p>A) resistive transducers → In these transducer resistance of sensing element changes in accordance with the physical quantity to be measured. eg. i) Potentiometer ii) strain gauge</p> <p>B) capacitive transducer → These transducers are used for the measurement of rotational motions with change in capacitance. This change in capacitance gets converted into an equivalent electrical signals eg. they are used for meas. of displacement, vibrations, pressure, sound, level etc.</p> <p>C) inductive transducers → They convert the displacement into change in inductance. It works on following principle. i) change in self inductance ii) change in mutual inductance.</p>	

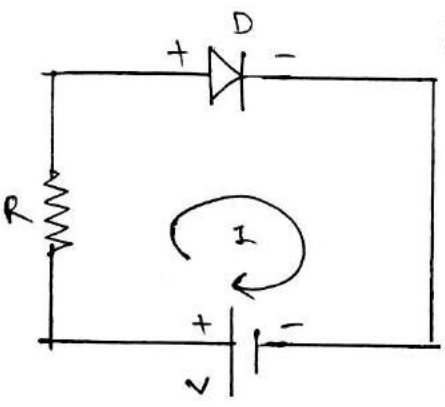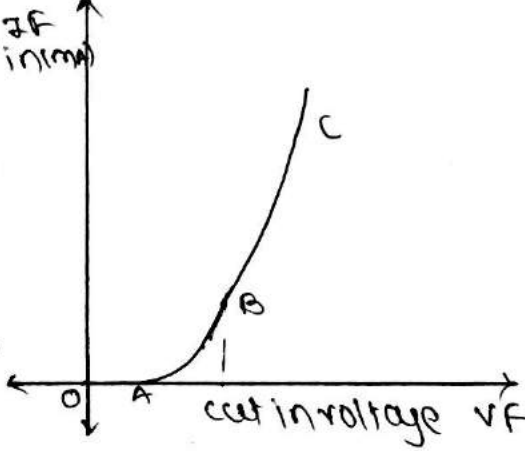SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	a)	<p>Draw the forward and Reverse characteristics of PN junction diode and explain it.</p> <p>Ans:</p>   <p>Fig. (a) Constructional diagram. Fig. (b) Forward chs.</p> <p>Fig (a) shows the constructional diagram of PN junction diode in forward biased and Fig (b) shows forward chs of PN junction diode. When positive terminal of battery is connected to P type semiconductor and negative terminal of battery is connected to N type semiconductor then the diode is said to be in forward biased. Due to negative terminal of battery connected to N region free electrons from N side are pushed towards P side</p>	<p>For diagram For ... 3 Marks</p> <p>For valid description 3M.</p>



SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	Q7	<p>similarly positive end of battery is connected to P region free holes from P region are pushed towards N side. with increase in battery supply voltage V more and more number of holes from P side & electrons from N side start travelling towards the junction</p> <p>A large No. of minority carriers crossing the junction constitute a current called forward current. Due to forward biasing the width of depletion region decreases and thus the potential barrier also decreases. as long as voltage V is less than potential barrier, the forward current does not flow but once the external voltage become equal to the barrier voltage (cut in voltage), the diode starts conducting and current increases as external voltage increases.</p> <p>Fig (b) shows the forward characteristics of PN junction diode. The relation between forward current and forward voltage is known as forward chs. of diode. The forward characteristics of diode is divided into two parts</p> <p>→ Region AB → Here in this region the forward voltage is small and less than cut in voltage</p>	


GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

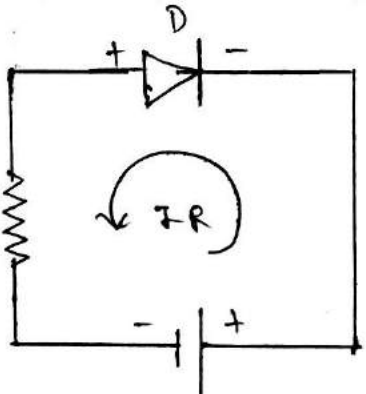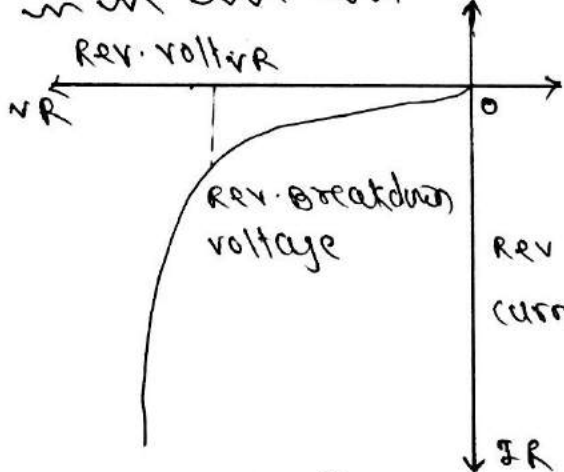SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	g)	<p>and width of depletion region goes on decreasing</p> <p>→ Region B to C → In this region B to C as soon as the forward voltage is equal to the cut in voltage of diode the current in the diode increases rapidly as shown in fig (b). cut in volt for Si = 0.7V and for Ge = 0.3V.</p> <p>Reverse biasing of PN junction diode →</p>  <p>Fig (c) Reverse biasing of PN junction diode</p>  <p>Fig (d) Reverse chs of PN junction diode</p>	

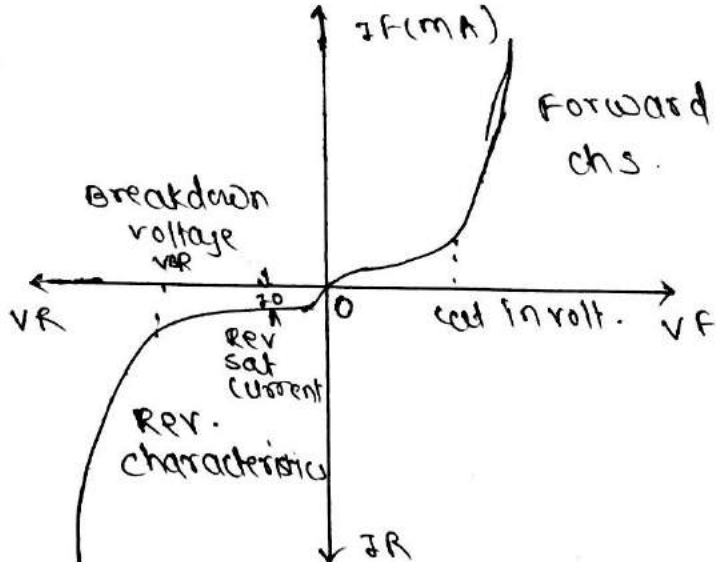
SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	a)	 <p>Fig ① <u>V-I chs of PN junction diode</u></p> <p>Fig ① shows the constructional diagram of PN junction diode in Reverse biased.</p> <p>Fig ② shows the Reverse ^{bias} characteristics of PN junction diode.</p> <p>If the P region of diode is connected to negative terminal of battery and N region is connected to the positive terminal of battery then the diode is said to be in Reverse biased. The Reverse current is denoted by I_R & flows from cathode to anode. When the diode is in Reverse bias, holes in P region are attracted towards negative terminal of supply and electrons</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

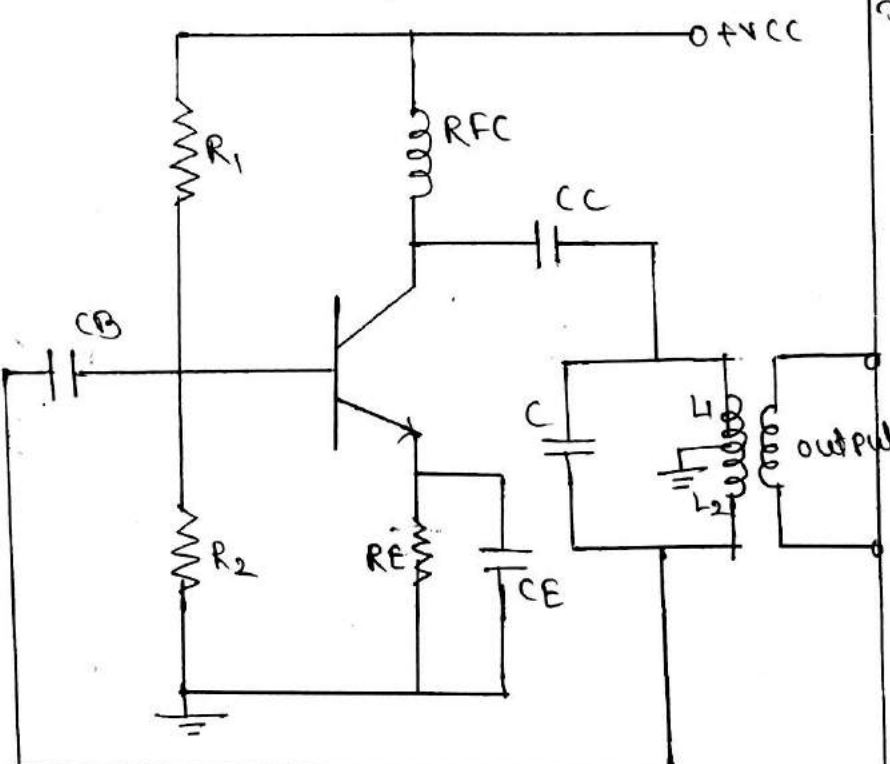SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	b) Ans:	<p>Draw the circuit and explain working principle of Hartley oscillator. state it's formula for frequency of oscillations.</p>  <p>Fig @ circuit diagram of Hartley oscillator</p> <p>Fig. @ shows the circuit of a Hartley oscillator. It consist of tank circuit of two coils L_1 and L_2 the coil L_1 is inductively</p>	<p>For correct diagram 3 Marks</p> <p>For valid explanation 2 M</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	b)	<p>coupled to coil L_2 and the combination works as an autotransformer. A coil called Radio frequency choke (RFC) is connected between collector and VCC supply. It acts as a load for the collector and also permits an easy flow of DC current but blocks AC current. The feedback between the output and input circuits is accomplished through autotransformer action which also introduces a phase shift of 180°. The transistor also introduces a phase shift of 180° therefore total phase shift is 360° and hence the feedback is positive.</p> <p>The capacitor C_C connected between collector and tuned circuit is called coupling capacitor. It permits only the AC currents to pass to the tank circuit. The capacitor C_B called blocking capacitor, further blocks the DC currents reaching the base. The resistors R_1, R_2, and R_E are used to provide DC bias to the transistor. When the circuit is energized by switching on the supply collector current flows</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105


SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	b)	<p>coupled to coil L_2 and the combination looks as an autotransformer. A coil called Radio frequency choke (RFC) is connected between collector and VCC supply. It acts as a load for the collector and also permits an easy flow of DC current but blocks AC current. The feedback between the output and input circuits is accomplished through autotransformer action which also introduces a phase shift of 180°. The transistor also introduces a phase shift of 180° therefore total phase shift is 360° and hence the feedback is positive.</p> <p>The capacitor C_C connected between collector and tuned circuit is called coupling capacitor. It permits only the AC currents to pass to the tank circuit. The capacitor C_B called blocking capacitor, further blocks the DC currents reaching the base. The resistors R_1, R_2, and R_E are used to provide DC bias to the transistor. When the circuit is energized by switching on the supply collector current flows</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105



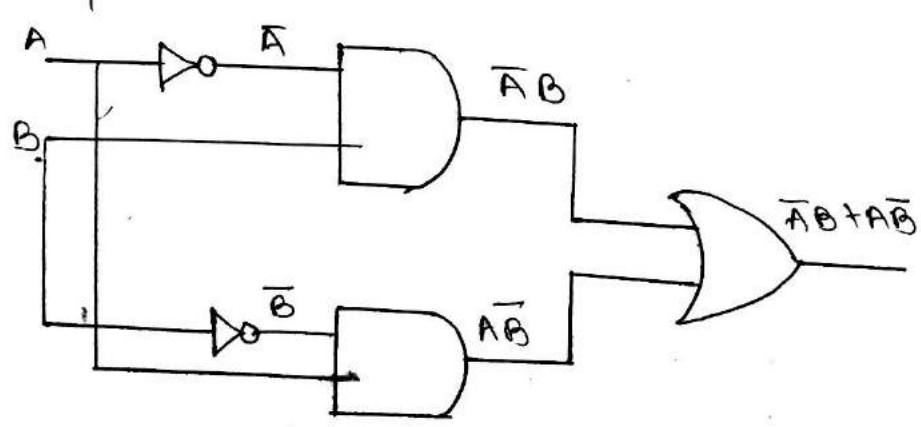
SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	b)	<p>The oscillations are produced because of positive feedback from the tank circuit. The frequency of oscillations is given by</p> $f_0 = \frac{1}{2\pi\sqrt{LC}}$ <p>Where $L = L_1 + L_2 + 2M$</p> $L = L_1 + L_2$ <p>(If the mutual inductance M is neglected)</p>	<p>For correct freq. formula 1 mark</p>
Q.2	<p>c)</p> <p>Ans:</p>	<p>Implement a digital circuit for logic equation using suitable gates.</p> <p>if $y = \bar{A}B + A\bar{B}$</p> 	<p>For correct implementation each 3M.</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

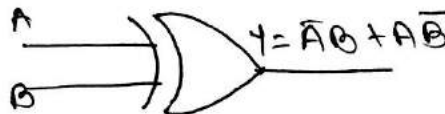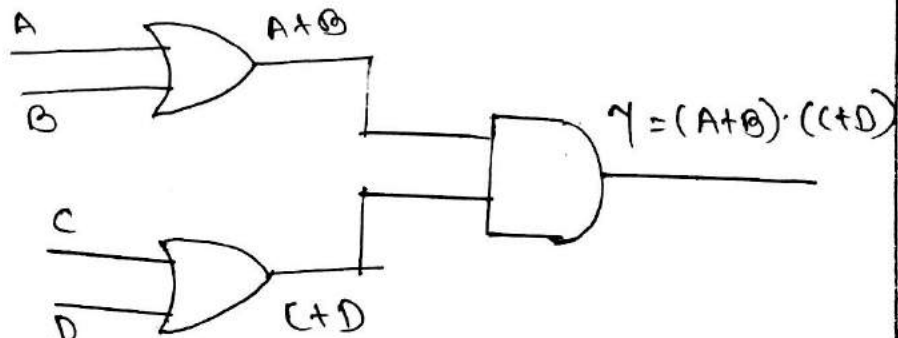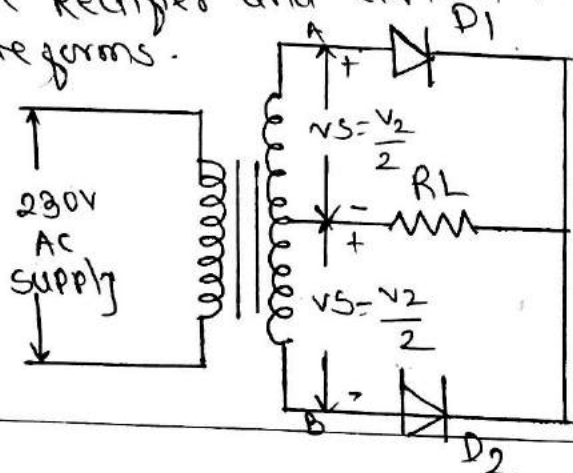SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.2	c)	<p>OR</p> <p>i) </p> <p>ii) $Y = (A+B) \cdot (C+D)$</p> <p></p>	
Q.3	a)	<p>Draw the circuit diagram of center tap full wave rectifier and explain it with its wave forms.</p> <p>Ans: </p> <p>Fig (a) Circuit diagram of center tap FWR</p>	<p>For correct circuit diagram 2 Marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.3	a)	<p>Fig. (b) I/P & o/p waveforms for centre tapped FWR</p>	<p>For correct waveforms & marks</p>


GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 8	a)	<p>Fig. (a) shows the circuit diagram of centre tap full wave rectifier. The circuit uses two diodes which are connected to the centre tapped secondary winding of transformer. The input signal is applied to the primary winding of the transformer. The centre tap on the secondary winding of a transformer is usually taken as the ground or zero voltage. The voltage across secondary winding (V_s) is divided into two parts, i.e. $\frac{V_s}{2}$ and $\frac{V_s}{2}$.</p> <p>During the positive half cycle when A is positive and terminal B is negative diode D_1 becomes forward biased and diode D_2 becomes reverse biased. As a result of this diode D_1 conducts and D_2 is off. so we will get o/p same as i/p.</p> <p>During the negative half cycle of i/p AC voltage when point A is negative and B is positive diode D_2 is forward biased and diode D_1 become reverse biased as a result of this diode D_1 is off and diode D_2 is on so current flows from diode D_2 Load Resistor to the sec. wdg.</p>	<p>For valid explanation or working 2 marks</p>

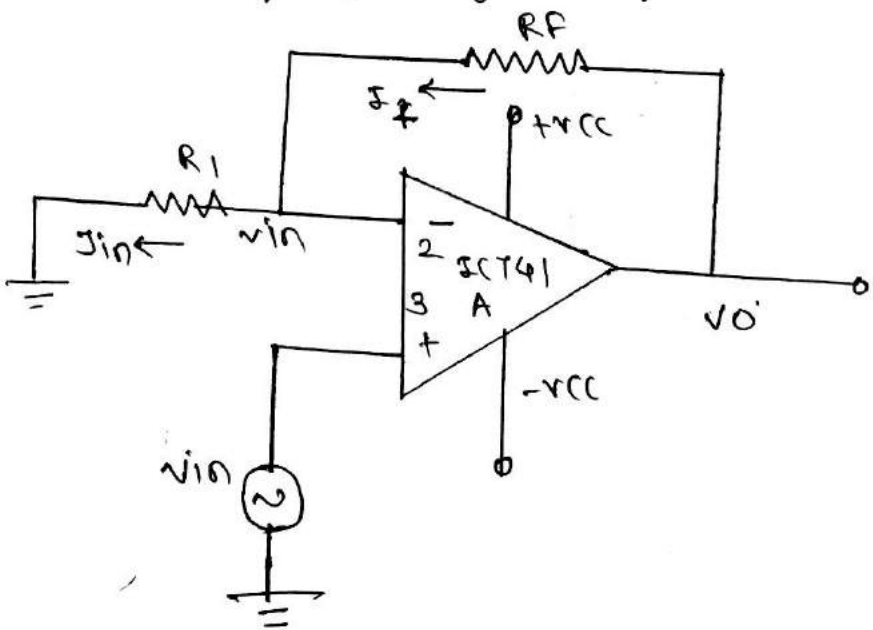SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 3	b)	<p>of transformer. so we will get full wave Rectified output during positive and negative half cycle as shown in fig (b).</p> <p>Draw the circuit diagram of op-amp as non inverting amplifier and also derive its expression for gain of Amplifier.</p> <p>Ans:</p>  <p>Fig. circuit diagram of op-amp as non inverting amplifier.</p>	<p>For correct diagram 3 Marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.3	b)	<p>By Kirchoff's current law</p> $I_F = I_{in}$ <p>Where $I_F = \frac{V_o - V_{in}}{R_F}$</p> <p>and $I_{in} = \frac{V_{in} - 0}{R_1}$</p> $\therefore \frac{V_o - V_{in}}{R_F} = \frac{V_{in} - 0}{R_1}$ $\frac{V_o - V_{in}}{R_F} = \frac{V_{in}}{R_1}$ $R_1 (V_o - V_{in}) = R_F V_{in}$ $R_1 V_o - R_1 V_{in} = R_F V_{in}$ $\therefore V_{in} (R_F + R_1) = V_o R_1$ $\therefore \frac{V_o}{V_{in}} = \frac{R_F + R_1}{R_1}$ $\therefore \boxed{ACL = 1 + \frac{R_F}{R_1}}$	<p>FOR expression derivation 3 MARKS.</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 3	<p>c)</p> <p>Ans:</p>	<p>Draw the block diagram of function generator and explain function of each block.</p> <p>Fig 1 Block diagram of function generator</p>	<p>For correct diagram 3 Marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q-3	c)	<p>Fig. (a) shows the block diagram of function generator. A function generator produces different waveforms of adjustable frequency. The common output waveforms are sine wave, square, triangular and sawtooth waves. usually the frequency is controlled by varying the capacitor in LC or RC circuit. In this instrument the frequency is controlled by varying the magnitude and of current which drives integrator. This instrument produces sine, triangular and square waves with frequency range of 0.01 Hz to 100 kHz.</p> <p>The frequency controlled voltage regulates two current sources. The upper current source supplies constant current to the integrator whose output voltage increases linearly with time, according to the equation of output signal voltage</p> $e_{out} = \frac{1}{C} \int_0^t i dt.$	<p>For valid explanation 3 marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.3	c7	<p>An increase or decrease in the current increases or decreases the slope of the output voltage and hence controls the frequency.</p> <p>The voltage comparator multivibrator changes state at a predetermined maximum level of the integrator output voltage. This change cuts off the upper current supply and switches on the lower current supply. The lower current source supplies a reverse current to the integrator, so that its o/p decreases linearly with time when the o/p reaches a predetermined minimum level the voltage comparator again change state and switches on the upper current source.</p> <p>The output of integrator is a triangular waveform whose frequency is determined by the magnitude of the current supplied by the constant current sources. The comparator o/p delivers a square wave volt. of same frequency.</p> <p>The resistance diode network alters the slope of the triangular wave its amplitude changes and produces a sine wave with less than 1% distortion.</p>	

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105


SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.3	c)	<p>An increase or decrease in the current increases or decreases the slope of the output voltage and hence controls the frequency.</p> <p>The voltage comparator multivibrator changes state at a predetermined maximum level of the integrator output voltage. This change cuts off the upper current supply and switches on the lower current supply. The lower current source supplies a reverse current to the integrator, so that its o/p decreases linearly with time when the o/p reaches a predetermined minimum level the voltage comparator again change state and switches on the upper current source.</p> <p>The output of integrator is a triangular waveform whose frequency is determined by the magnitude of the current supplied by the constant current sources. The comparator o/p delivers a square wave volt. of same frequency.</p> <p>The resistive diode network alters the slope of the triangular wave it's amplitude changes and produces a sine wave with less than 1% distortion.</p>	

GOVERNMENT POLYTECHNIC, PUNE


MODEL ANSWERS AND MARKING SCHEME(ODD 2019)


COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

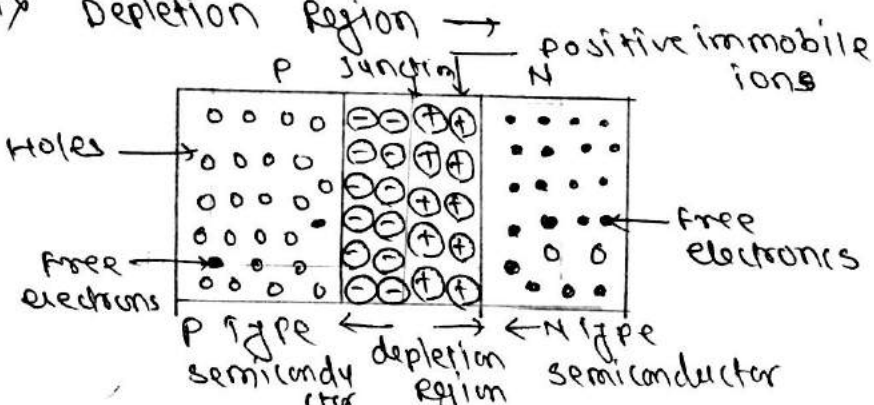SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	<p>Q.4</p> <p>Ans:</p>	<p>Explain the following Terms.</p> <p>i) cut in voltage → A minimum voltage applied to a forward biased diode at which current starts increasing rapidly called as cut in voltage. for Si = 0.6V, Ge = 0.3V</p> <p>OR</p> <p>cut in voltage is also define as the voltage at which forward current starts increasing rapidly.</p> <p>ii) Depletion Region →</p>  <p>Fig. (a) P-N junction diode with depletion region.</p> <p>At the instant of PN junction formation, the free electrons near the junction in the N region begin to diffuse across the</p>	<p>For each correct defn 2 marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	a)	<p>junction into the p-region where they combine with holes near the junction. The result is that n region loses the free electrons as they diffuse into the junction. This creates a layer of positive charge (pentavalent ions) near the junction. As the electrons move across the junction, the p region loses holes as the electrons and holes combine. The result is that there is layer of negative charges near the junction. These two layers of positive and negative charges form the depletion region. Depletion region contains only immobile ions and no free charge carriers.</p> <p>iii) Junction capacitance \rightarrow junction capacitance is the capacitance which forms in a pn junction diode under reverse bias. When reverse biased voltage applied across pn junction diode, the holes from p-type region moves away from junction</p>	

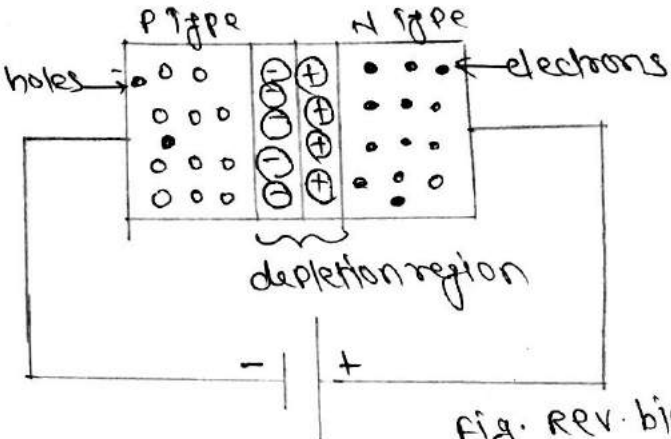SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	a)	<p>Here the width of depletion region ^{increases if} acts a dielectric medium and two electrodes store the electric charge.</p>  <p>When the voltage applied to PN junction increases the depletion region will increase. so the size of P & N region is decreased. consequently the ability to store electric charge will be reduced. The PN junction diode with more narrow depletion width & large at junction can store more electric charge.</p>	

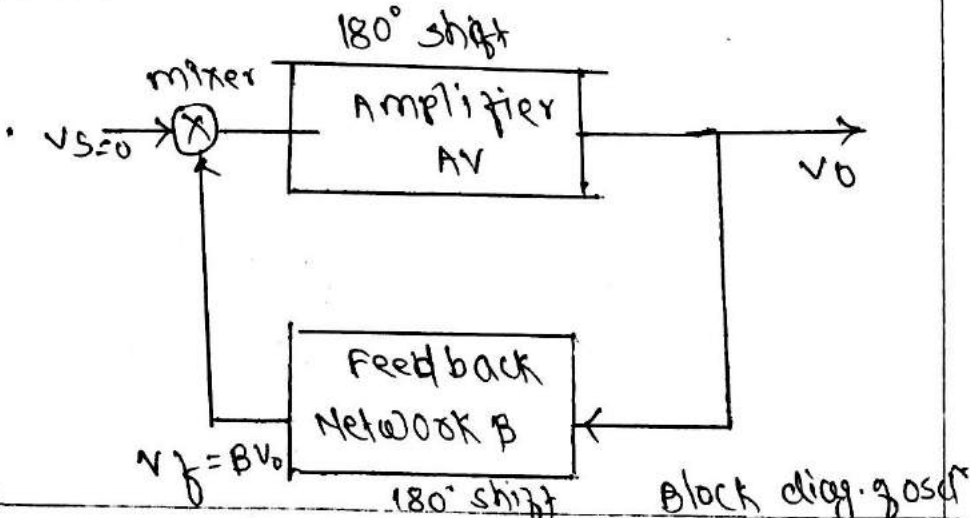SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	b)	<p>Define oscillator. state and explain Barkhausen criteria for sustained oscillator.</p> <p>Ans: oscillator is a device which produces an output signal, without any i/p signal of any desired frequency.</p> <p>Barkhausen criteria → An amplifier will work as oscillator if and only if it satisfies a set of conditions called Barkhausen criteria</p> 	<p>For definition 2 MARKS</p> <p>For correct explanation 4 MARKS</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 6	b)	<p>For an oscillator circuit there is no i/p signal v_s hence the feedback signal v_f itself should be sufficient to maintain the oscillations.</p> <p>Barkhausen criteria is that in order to produce continuous undamped oscillations at the o/p of an amplifier the positive feedback should be $\beta \cdot A_V = 1$</p> <p>The overall volt gain of the feedback amplifier is given by</p> $A_V' = \frac{A_V}{1 - \beta \cdot A_V}$ <p>where</p> <p>A_V = gain of an amplifier without feedback</p> <p>$\beta \cdot A_V$ = product of feedback fraction and open loop gain</p> <p>In order to produce positive feedback the feedback network must provide a phase shift of 180° between the i/p and output signals.</p>	

GOVERNMENT POLYTECHNIC, PUNE


MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	b)	<p>and 180° phase is provided by amplifier so as to provide a signal with a phase shift of 360° or 0° at the amplifier input.</p> <p>The above two condition for positive feedback (i.e $\beta \cdot A_V = 1$ and the net phase shift around the loop equal to 360° or 0°) are called Barkhausen criteria for oscillations. mathematically. Barkhausen criteria is also stated as</p> $\beta \cdot A_V = 1$ $\angle \beta \cdot A_V = 0^\circ$	
Q.4	c)	<p>state and explain selection criteria of transducer (any six)</p> <p>Ans: 1) operating principle - transducer is selected on the basis of operating principle used may be resistive, capacitive inductive</p>	<p>For each correct criteria 1 MARK</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	c)	<p>2) Loading effect - The transducer should be selected such that it should not affect the value of the parameter under measurement</p> <p>3) Environmental considerations → while selecting the transducers it is necessary to consider the environmental parameters like humidity, shocks, vibrations, corrosion, moist.</p> <p>4) Errors → Transducer should maintain the expected i/p and output relationship as described by its transfer function so as to avoid errors.</p> <p>5) Accuracy → It should work with high degree of accuracy under operating conditions. Calibration and repeatability are the important parameters for good accuracy</p> <p>6) Simplicity, Reliability and low maintenance → A transducer should be selected its simplicity, reliability and maintenance cost.</p>	

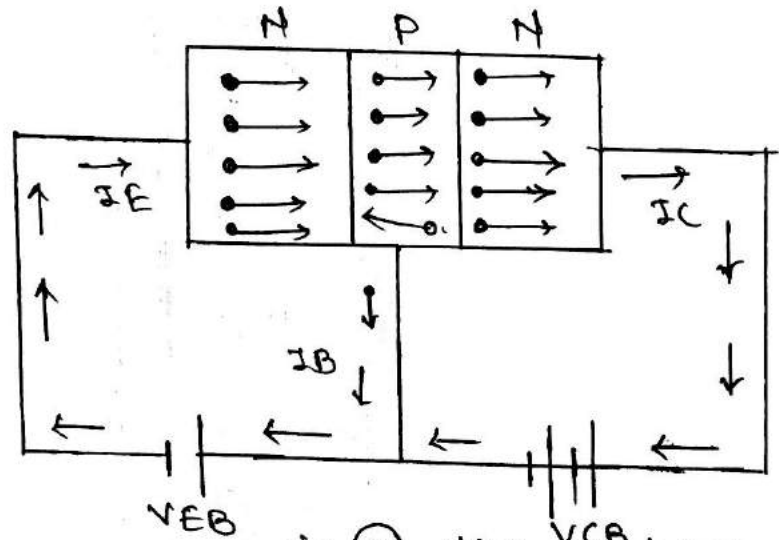SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.4	C	<p>7) Time span → The time span indicates the time period for which a transducer works reliably. according to application transducers should be selected so that it will work properly for the desired time span.</p> <p>8) Cost and availability → general factors involved in selection are cost and availability</p>	
Q.5	a)	<p>Draw and explain working of NPN transistor.</p> <p>Ans:</p>  <p>Fig (Q) NPN transistor</p>	<p>For valid diagram 3 marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.5	Q7	<p>Fig @ shows circuit diagram for NPN transistor with forward bias to base emitter junction and Reverse bias to base collector junction. The forward bias causes the electrons in the N type emitter to flow towards the base. This constitutes the emitter current I_E As these electrons flow through P type base, they tend to combine with holes. As the base is lightly doped and very thin therefore only a few electrons (less than 5%) combine with holes. to constitute base current I_B the remaining 95% of electrons cross over into the collector region to constitute collector current I_C. In this way almost entire emitter current flows in the collector circuit. ^{so sum of} the collector current and base current is equal to the emitter current. It is given by</p> $I_E = I_B + I_C$	<p>For explanation 3 MARKS</p>


GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME (ODD 2019)



COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105


SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME												
Q. 5	b)	<p>ii) determine the decimal number represented by given binary number</p> <p>Ans: $(1101.0101)_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 0 \times 2^{-1} + 1 \times 2^{-2} + 0 \times 2^{-3} + 1 \times 2^{-4}$</p> $= 8 + 4 + 0 + 1 + 0 + \frac{1}{4} + 0 + \frac{1}{16}$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $(1101.0101) = (13.3125)_{10}$ </div> <p>ii) convert $(247)_{10}$ into octal</p> <table style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th></th> <th>Quotient</th> <th>Remainder</th> </tr> </thead> <tbody> <tr> <td>$\frac{247}{8}$</td> <td>30</td> <td>7</td> </tr> <tr> <td>$\frac{30}{8}$</td> <td>3</td> <td>6</td> </tr> <tr> <td>$\frac{3}{8}$</td> <td>0</td> <td>3</td> </tr> </tbody> </table> <p style="text-align: center;">$(247)_{10} = (367)_8$</p>		Quotient	Remainder	$\frac{247}{8}$	30	7	$\frac{30}{8}$	3	6	$\frac{3}{8}$	0	3	<p>For correct answer 3 Mark each.</p>
	Quotient	Remainder													
$\frac{247}{8}$	30	7													
$\frac{30}{8}$	3	6													
$\frac{3}{8}$	0	3													

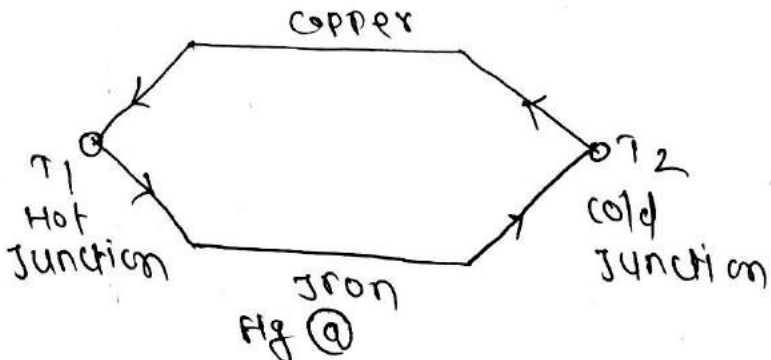SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.5	c) Ans:	<p>Explain working principle of Thermocouple</p> <p>Thermocouple is a thermoelectric transducer which convert thermal energy into an electrical energy. Thermocouple is used as primary transducer for temperature measurement in which change in temperature are directly converted into an electrical signal.</p>  <p>seebeck effect → In 1821 the great scientist Prof seebeck discovered that if the two wires of different metals are joined together forming closed circuit and if two are junctions formed are at different temperature, an electric current flow around a closed circuit this is called seebeck effect</p>	<p>For diagram 2 Marks</p> <p>For explanation 4 Marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.5	c)	<p>He also observed that if the two metals used are copper and iron, then the current flows from copper to iron at hot junction and from iron to copper at cold junction as shown in fig (a)</p> <p>If the copper wire is cut then emf appears across the open circuit as shown this emf is commonly known as seebeck emf. This emf is proportional to the difference in the temperature of the two junction. A thermocouple consists of a pair of dissimilar metal wires joined together at one end, forming a hot junction and terminated at the other end known as reference or cold junction. When heat is applied to the hot junction a temperature difference exists between the hot & cold junction causing generation of emf. The magnitude of this emf depends on the material used for the wires and the temperature difference between the two junctions.</p>	

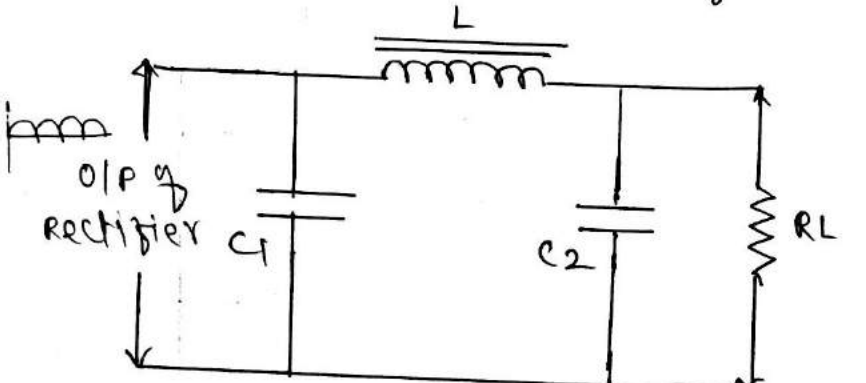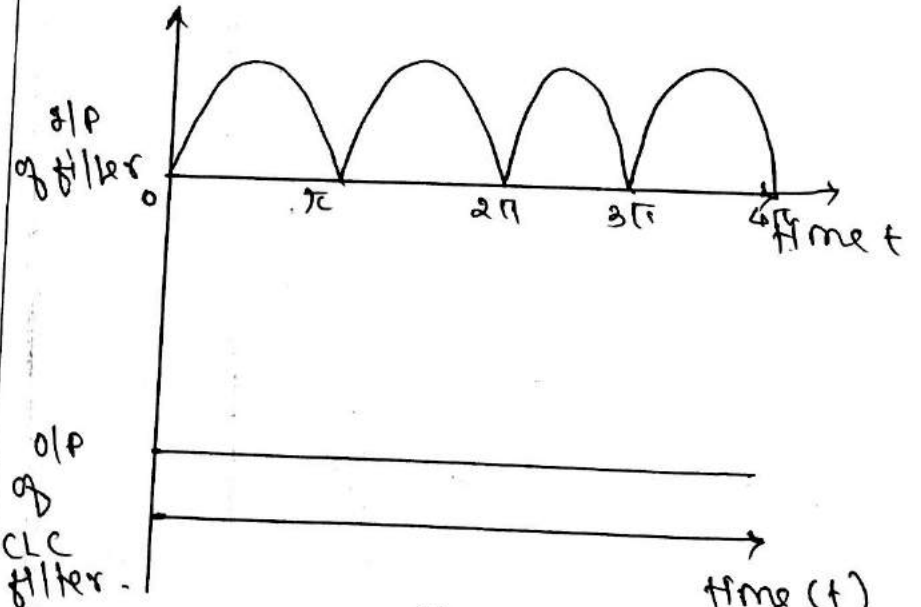SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.6	Q.6	<p>Draw and explain working of π filter with its input and output waveforms</p> <p>Ans:</p>  <p>Fig (a) circuit diagram</p>  <p>Fig (b) I/P & O/P waveforms</p>	<p>For correct circuit diagram 2 marks</p> <p>For correct waveforms 2 marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.6	a)	<p>Fig (a) shows the circuit diagram of π filter and (b) shows the fil & olp waveforms for π filter.</p> <p>A filter which uses two capacitor and one inductor is called CLC filter or π filter. It consist of two capacitor C_1 & C_2 which is connected in shunt & one inductor L connected in series betⁿ two capacitors.</p> <p>The olp of rectifier is connected as input to capacitor C_1. capacitor C_1 offers low low reactance to ac component of rectifier olp but it offers infinite reactance to dc component so C_1 bypasses ac component and blocks dc component. Inductor offers a high reactance to ac component of rectifier output but zero reactance to the dc component therefore it allows the dc component to pass through it and blocks the ac component which could not be bypassed by capacitor C_1.</p> <p>capacitor C_2 bypasses the ac component of rectifier output which could not be blocked by inductor L as result of this we will get pure dc olp.</p>	for valid working 2 marks

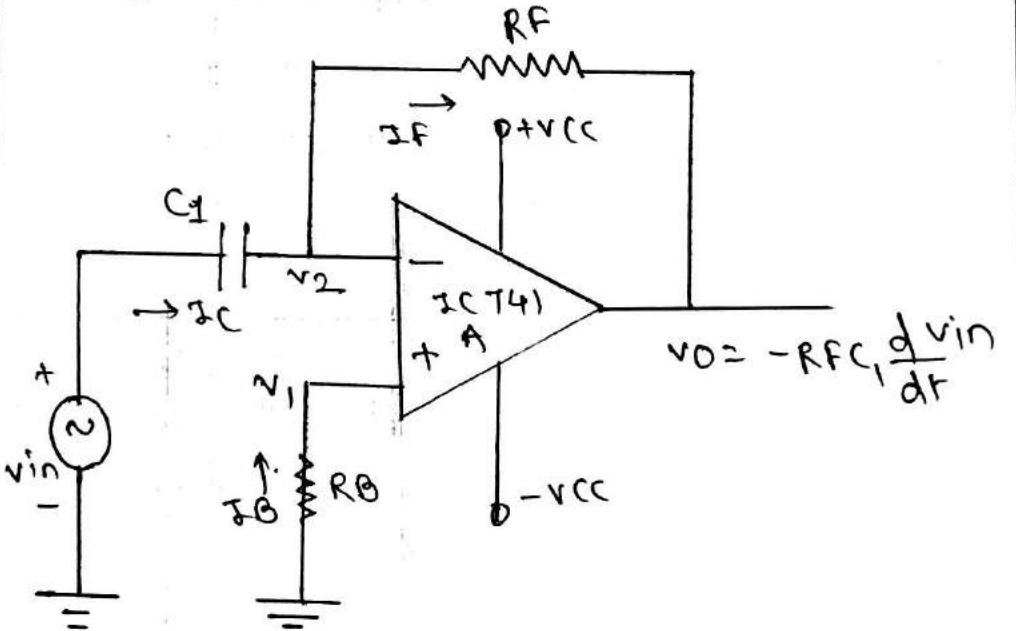SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q. 6	b)	<p>Draw the circuit diagram of op-amp as differentiator and explain it with it's output expression.</p> <p>Ans:</p>  <p>Fig: circuit diagram of op-amp as differentiator</p> <p>Derivation →: by KCL</p> $I_C = I_B + I_F$ <p>but $I_B \approx 0$</p> $\therefore I_C = I_F$	<p>For correct diagram 3 Marks</p> <p>For derivation 3 Marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.6	b)	<p>The basic relation between current through and voltage across capacitor is given by</p> $I_C = C \frac{dV_C}{dt}$ $\therefore I_C = C_1 \frac{dV_C}{dt} \quad \text{--- (1)}$ <p>The voltage across C_1 is given by</p> $V_C = V_{in} - V_2$ <p>Put the value of V_C in eqn (1)</p> $\therefore I_C = C_1 \frac{d(V_{in} - V_2)}{dt}$ <p>Now let us obtain the expression for current I_F</p> $I_F = \frac{V_2 - V_0}{R_F}$ <p>but I_C & I_F are equal from eqn (1)</p>	

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.6	b)	$C_1 \frac{d}{dt}(v_{in} - v_2) = \frac{v_2 - v_o}{R_F} \quad \text{--- (3)}$ <p>by virtual ground concept $v_1 = v_2 = 0$ put this value in eqⁿ (3)</p> $\therefore \frac{C_1 d}{dt}(v_{in} - 0) = \frac{0 - v_o}{R_F}$ $\therefore C_1 \frac{d}{dt} v_{in} = -\frac{v_o}{R_F}$ $\therefore \boxed{v_o = -R_F C_1 \frac{d}{dt} v_{in}}$ <p>thus the o/p voltage is differentiation of i/p voltage.</p>	

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
Q.6	c) Ans:	<p>Draw the block diagram of CRO and states any four Applications of CRO</p> <p>FIG: Block diagram of CRO.</p>	<p>For correct diagram 3 Marks</p>

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
		<p>Four Application of CRO are as follows.</p> <p>i) In Laboratory: → CRO can be used in laboratory for the measurement of AC/DC voltage, AC/DC current, frequency, phase.</p> <p>ii) In Radar → CRO is used in radar for giving the visual indication of target such as aeroplane, ship etc.</p> <p>iii) In Television → In TV Receiver a CRT along with associated sweep circuit is used for the creation of image, on the CRT picture tube.</p> <p>iv) In Medical science → CRO is used in Electrocardiogram (ECG), Electromyogram (EMG) and Electroencephalogram (EEG). The ECG is used for the diagnosis of heart condition of patient. EEG is used to study the brain condⁿ of patient.</p>	<p>For correct Applications (2M) each Applⁿ 1/2 marks</p>

GOVERNMENT POLYTECHNIC, PUNE

MODEL ANSWERS AND MARKING SCHEME(ODD 2019)

COURSE NAME: ELEMENTS OF ELECTRONICS ENGINEERING

COURSE CODE: ET2105

SR.NO	SUB QUE.	MODEL ANSWERS	MARKING SCHEME
		<p>v) In Radio Work \rightarrow CRO is used to trace and measure a signal throughout the RF, and AF channels of Radio and Television Receiver</p> <p>vii) In Industry \rightarrow CRO is used in Electronic industry for measurement of AC/DC voltage across different components of working circuit.</p>	